



uStomp.com - Ibanez TS-808

It's the tube screamer. Considered by many to be the overdrive pedal.

Transistors should be low noise NPN 2N5088 or 2N3904

IC should be a 4558

Diodes should be 1N914's

Layout and presentation © 2003 Steven Rittmeyer.
 All rights reserved. Authorization for personal use only.
 Any commercial use is forbidden.
 Permission for posting/serving limited to <http://www.ustomp.com>
 Permission refused for serving from or posting to other sites.